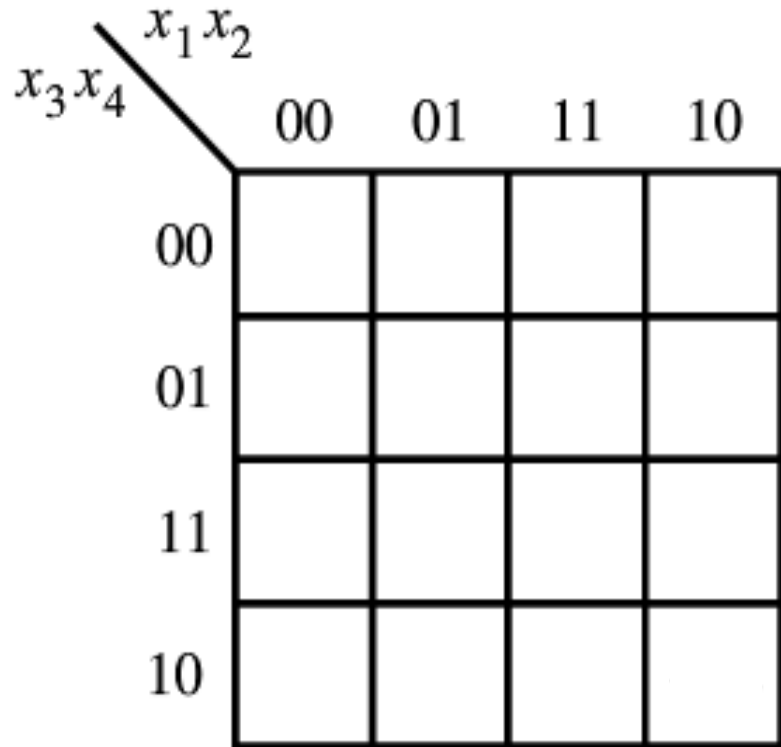


# Chapter 3 cont

# Where we left off

- 4 variable maps.



# 5 Variable Maps

NOT in your Book

Basically use 2 4-variable maps AND label each with the 5th variable.

$$F = z + z'(v'w + xy)$$

Get the Sum of Products

$$F = z + v'wz' + xyz' \quad \text{distribution}$$

Two ways to attack this

create the truth table then the K-Map

or just fill in the K-Map


$$F = z + v'wz' + xyz'$$

v	w	x	y	z	F	v	w	x	y	z	F
0	0	0	0	0		1	0	0	0	0	
0	0	0	0	1		1	0	0	0	1	
0	0	0	1	0		1	0	0	1	0	
0	0	0	1	1		1	0	0	1	1	
0	0	1	0	0		1	0	1	0	0	
0	0	1	0	1		1	0	1	0	1	
0	0	1	1	0		1	0	1	1	0	
0	0	1	1	1		1	0	1	1	1	
0	1	0	0	0		1	1	0	0	0	
0	1	0	0	1		1	1	0	0	1	
0	1	0	1	0		1	1	0	1	0	
0	1	0	1	1		1	1	0	1	1	
0	1	1	0	0		1	1	1	0	0	
0	1	1	0	1		1	1	1	0	1	
0	1	1	1	0		1	1	1	1	0	
0	1	1	1	1		1	1	1	1	1	


$$F = z + v'wz' + xyz'$$

v	w	x	y	z	F
0	0	0	0	0	0
0	0	0	0	1	1
0	0	0	1	0	0
0	0	0	1	1	1
0	0	1	0	0	0
0	0	1	0	1	1
0	0	1	1	0	1
0	0	1	1	1	1
0	1	0	0	0	1
0	1	0	0	1	1
0	1	0	1	0	1
0	1	0	1	1	1
0	1	1	0	0	1
0	1	1	0	1	1
0	1	1	1	0	1
0	1	1	1	1	1

$$F = z + z'(v'w + xy)$$

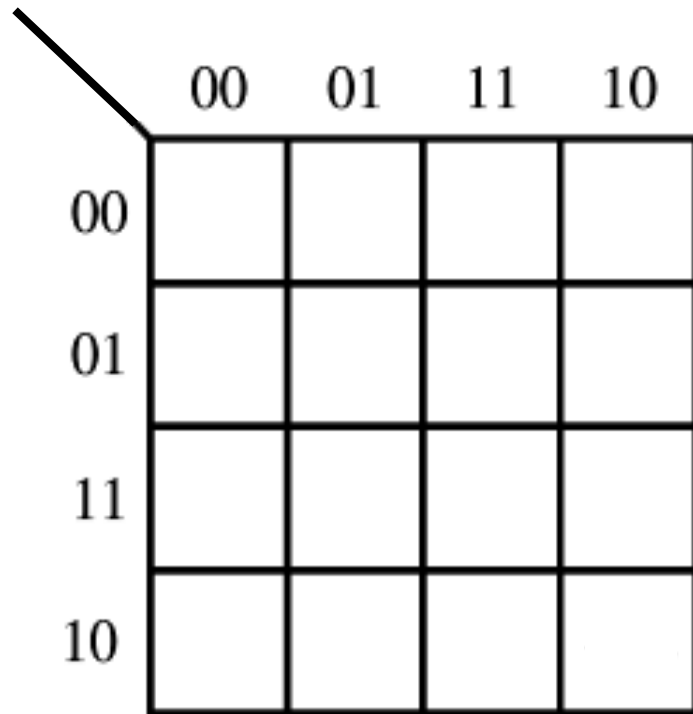


	00	01	11	10
00				
01				
11				
10				

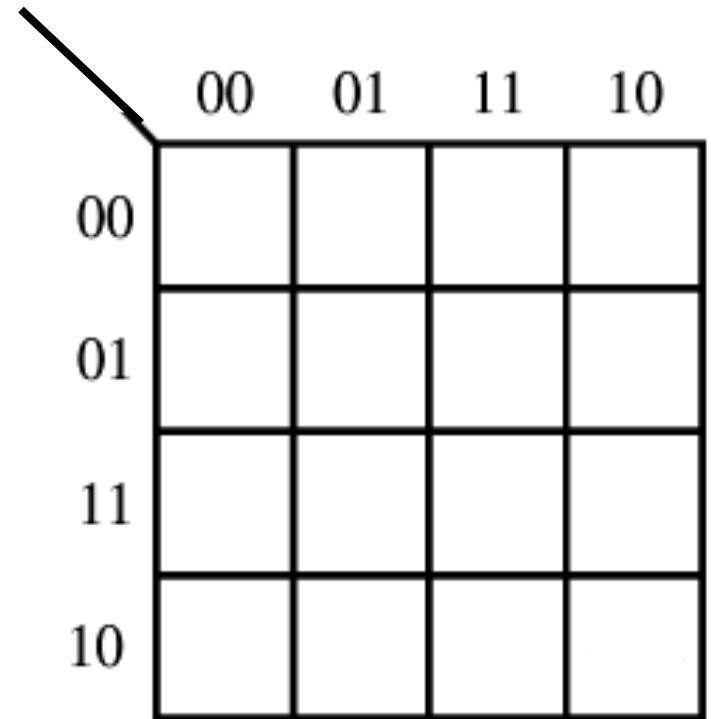

	00	01	11	10
00				
01				
11				
10				

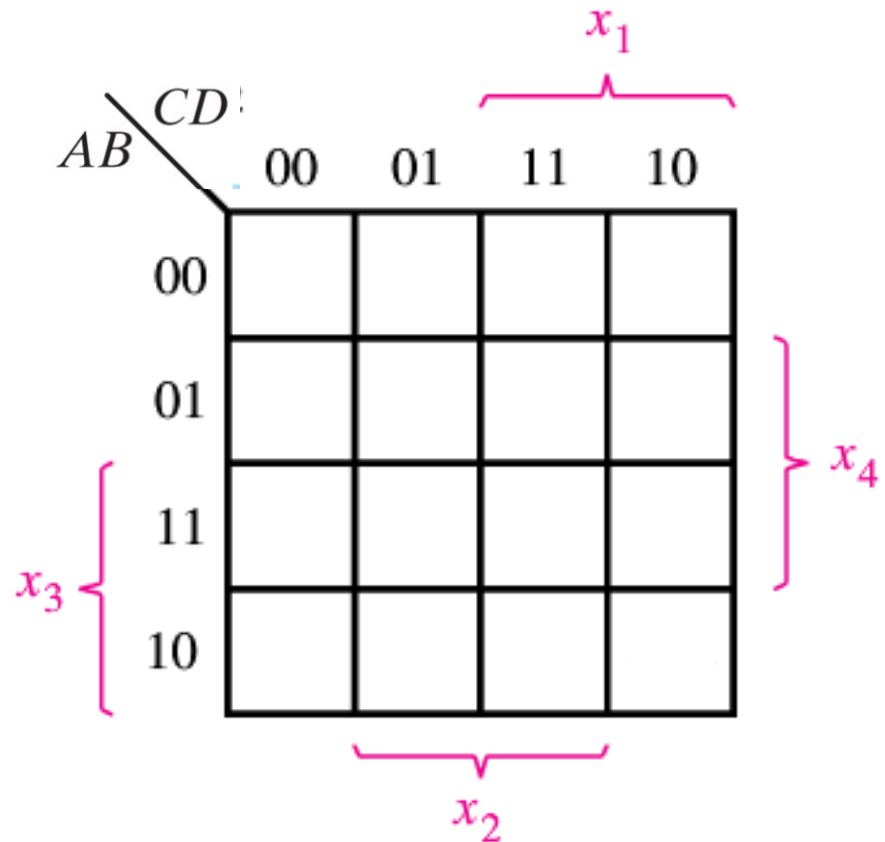
# Product of Sums


$$F(A, B, C, D) = \sum(0, 1, 2, 5, 8, 9, 10)$$





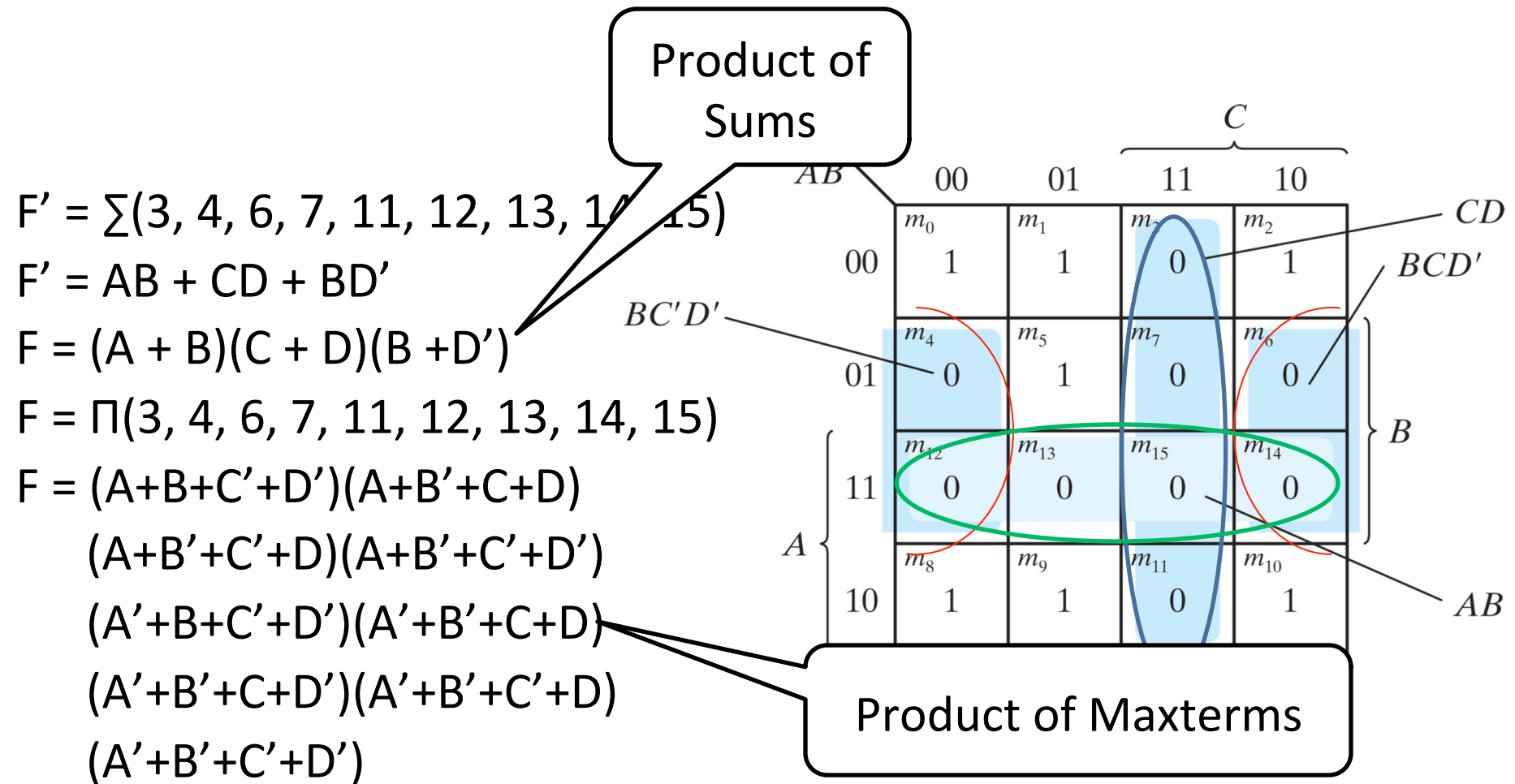
$$F(A, B, C, D) = \sum(0, 1, 2, 5, 8, 9, 10)$$



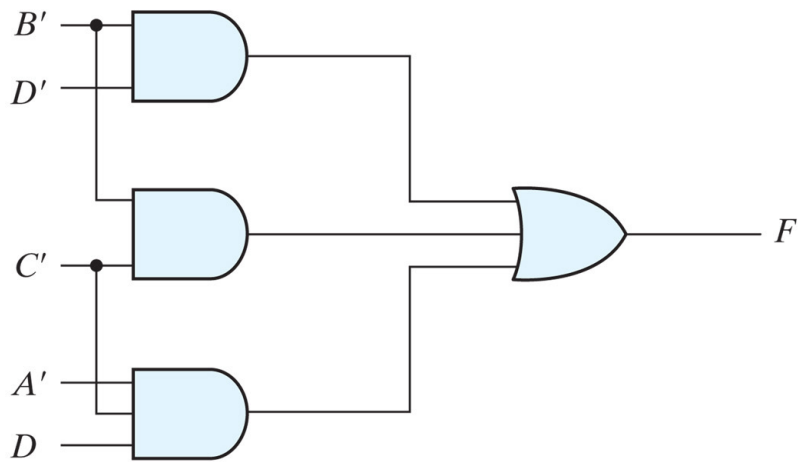

(a)  $F = B'D' + B'C' + A'C'D$

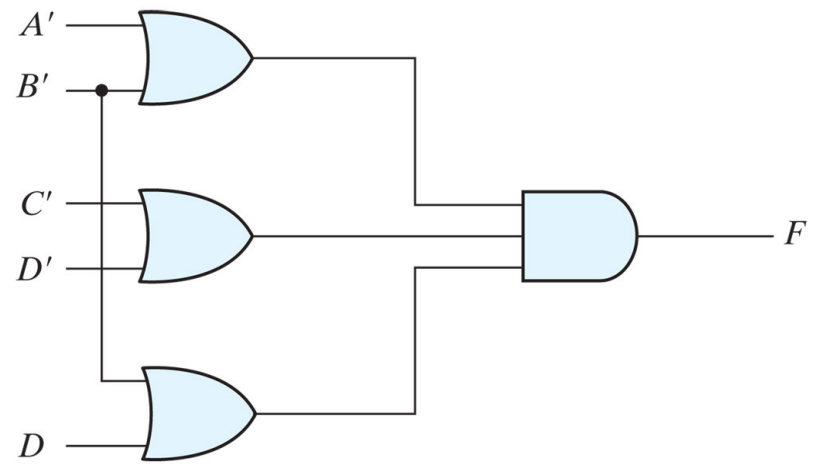


(b)  $F = (A' + B')(C' + D')(B' + D)$

# Don't Cares

- *Incompletely specified functions*
  - A function which has an output which is unspecified for a given set of inputs.
- Don't care conditions
  - The unspecified minterms of a function.

$$F(w, x, y, z) = \Sigma(1, 3, 7, 11, 15)$$

$$d(w, x, y, z) = \Sigma(0, 2, 5)$$

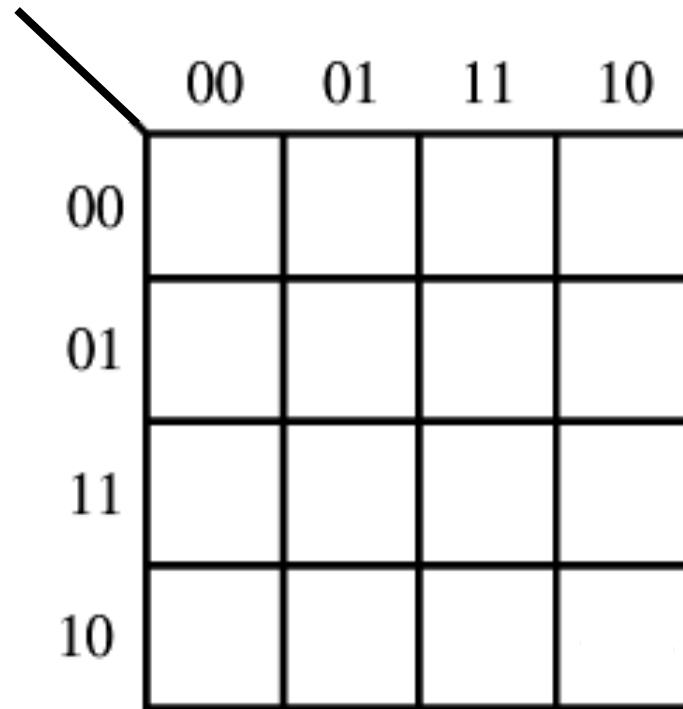

A 4x4 Karnaugh map grid. The columns are labeled 00, 01, 11, 10 from left to right. The rows are labeled 00, 01, 11, 10 from top to bottom. A diagonal line is drawn from the top-left corner of the grid to the top-left corner of the first cell.

	00	01	11	10
00				
01				
11				
10				

- $F(x,y,z) = \Sigma(0, 2, 4, 5)$

$$F(x, y, z) = x'y' + yz + x'yz'$$

$$F(A, B, C, D) = \Sigma(3, 7, 11, 13, 14, 15)$$




- $F(A, B, C, D) = \prod(1, 3, 5, 7, 13, 15)$




# NAND and NOR implementations


- Digital circuits are generally built using NAND and NOR.
- Why? Because they're easier to make.
- The basic gates used in all IC digital logic circuits
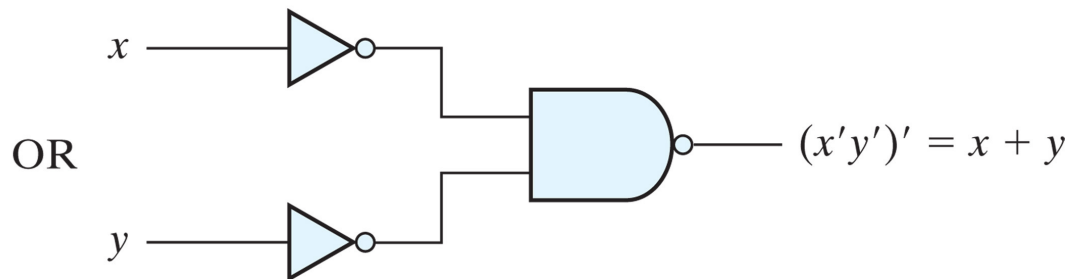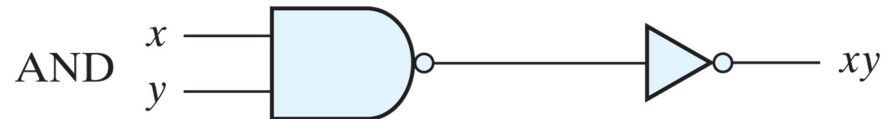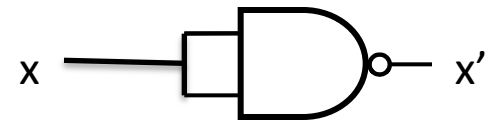
# The 3 basic functions (NOR, AND, and OR) from a NAND.



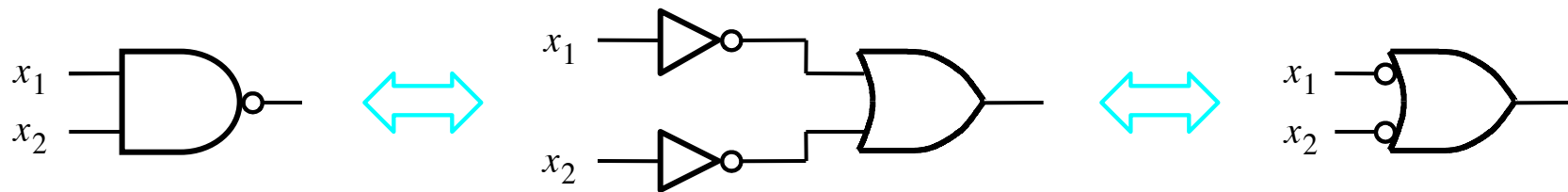

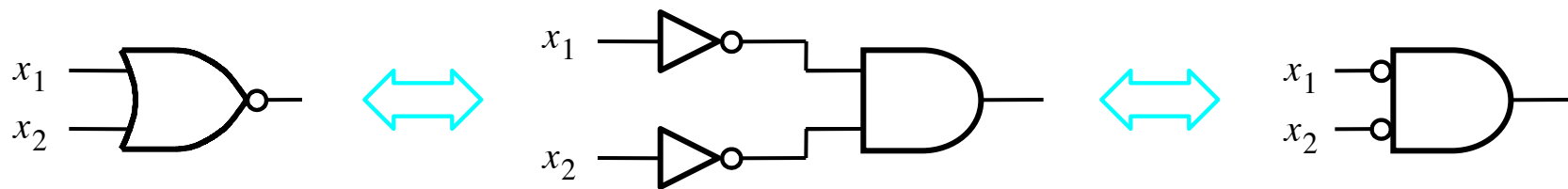(a)  $\overline{x_1 x_2} = \bar{x}_1 + \bar{x}_2$



(b)  $\overline{x_1 + x_2} = \bar{x}_1 \bar{x}_2$

