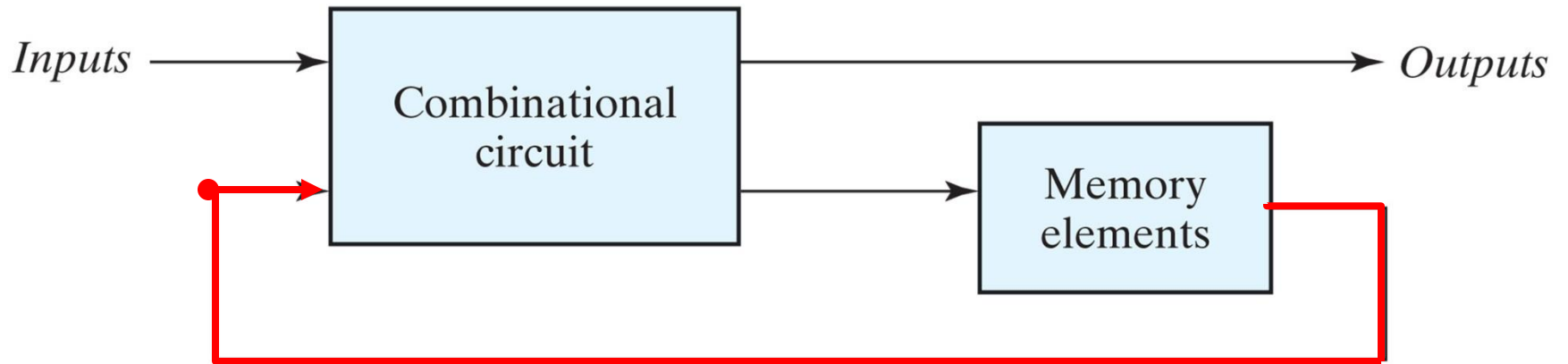


# Chapter 5

# Sequential Circuits

- Combinational vs Sequential
- Its all about feedback
- What is feedback?
  - The output of a circuit acts as an input to the circuit

# Feedback



- Combinational
  - No feedback
  - Output depends solely on the inputs
- Sequential
  - Feedback
  - Current state depends on previous state
- State
  - Output at a given time
  - State is tied to a specific point in time

# Sequential Circuits


- Feedback allows for the creation of a storage element.
  - Memory
  - Store, retain, and retrieve information

- Thus a sequential circuit is specified by a time sequence of inputs, outputs, and internal states.
- Two main types of sequential circuits
  - Synchronous
  - Asynchronous

- Synchronous
  - Behavior of the circuit is defined by the knowledge of its signals at a discrete points in time
- Asynchronous
  - Behavior depends on the inputs at ANY instant in time AND the order in which the inputs change

 - Asynchronous
  - Can be thought of as a combinational circuit with feedback
  - Can become unstable due to feedback among gates
- Synchronous
  - Uses a clock generator or clock
  - Determines when computational activity will occur within the circuit.





(a) Block diagram



(b) Timing diagram of clock pulses

# Storage Elements

- Latches vs Flip-flops
  - Latch - A change in signal level changes output
  - Flip-flop – Controlled by the transition from high to low or low to high NOT the level.




# Latches

- Useful for storing binary information and for the design of asynchronous circuits
- Not practical for use as storage elements in sequential circuits

# SR Latch

- SR – Set/Reset

 

(a) Logic diagram

$S$	$R$	$Q$	$Q'$
1	0	1	0
0	0	1	0
0	1	0	1
0	0	0	1
1	1	0	0


(b) Function table

$Q = 1$  &  $Q' = 0$   
Latch is set

Note: 00 results  
in no change on  
the output.

$Q = 0$  &  $Q' = 1$   
Latch is reset

- Can also build with NAND Gates

 


(a) Logic diagram

$S$	$R$	$Q$	$Q'$
1	0	0	1
1	1	0	1
0	1	1	0
1	1	1	0
0	0	1	1

(b) Function table

# SR-Latch with Enable

 


(a) Logic diagram

$En$	$S$	$R$	Next state of $Q$
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$ ; reset state
1	1	0	$Q = 1$ ; set state
1	1	1	Indeterminate

(b) Function table
 
# D-Latch




- Eliminates the indeterminate condition of the SR-Latch



(a) Logic diagram

$En$	$D$	Next state of $Q$
0	X	No change
1	0	$Q = 0$ ; reset state
1	1	$Q = 1$ ; set state

(b) Function table

   





# Flip-flops

- A binary storage device capable of storing 1 bit of binary information.
- Used in clocked sequential circuits
- State is changed by a change in the control input
  - Clock transition
  - A trigger

# Edge-Triggered D Flip-flop

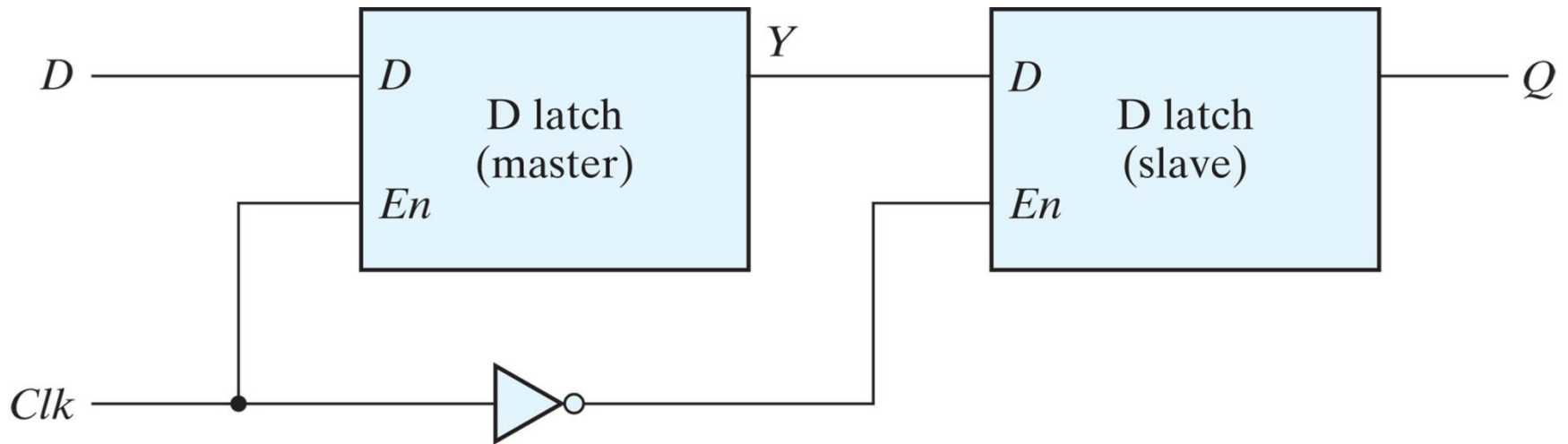


# D-type Positive Edge Triggered F/F

 


# D-Flip-flop

**D Flip-Flop**

<b><i>D</i></b>	<b><math>Q(t + 1)</math></b>
0	
1	

 


(a) Positive-edge

 


(a) Negative-edge


# JK Flip-Flop

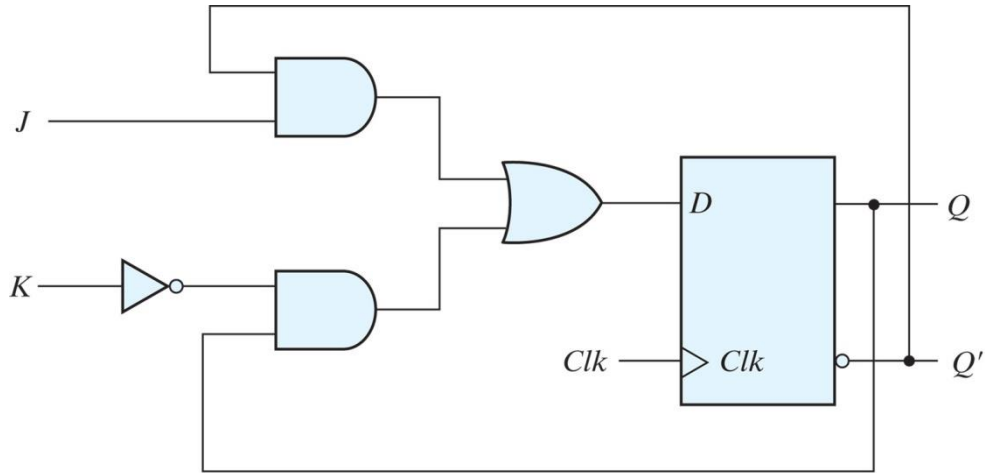

JK Flip-Flop		
$J$	$K$	$Q(t + 1)$
0	0	
0	1	
1	0	
1	1	

 


# Toggle Flip-Flop

 

**T Flip-Flop**


<b><math>T</math></b>	<b><math>Q(t + 1)</math></b>
0	
1	

 

# Make a T from a JK

<b><i>JK</i> Flip-Flop</b>		
<b><i>J</i></b>	<b><i>K</i></b>	<b><math>Q(t + 1)</math></b>
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$Q'(t)$

<b><i>T</i> Flip-Flop</b>	
<b><i>T</i></b>	<b><math>Q(t + 1)</math></b>
0	$Q(t)$
1	$Q'(t)$

 

# From a D Flip-flop

**D Flip-Flop**

<b><math>D</math></b>	<b><math>Q(t + 1)</math></b>
0	0
1	1

**T Flip-Flop**

<b><math>T</math></b>	<b><math>Q(t + 1)</math></b>
0	$Q(t)$
1	$Q'(t)$

