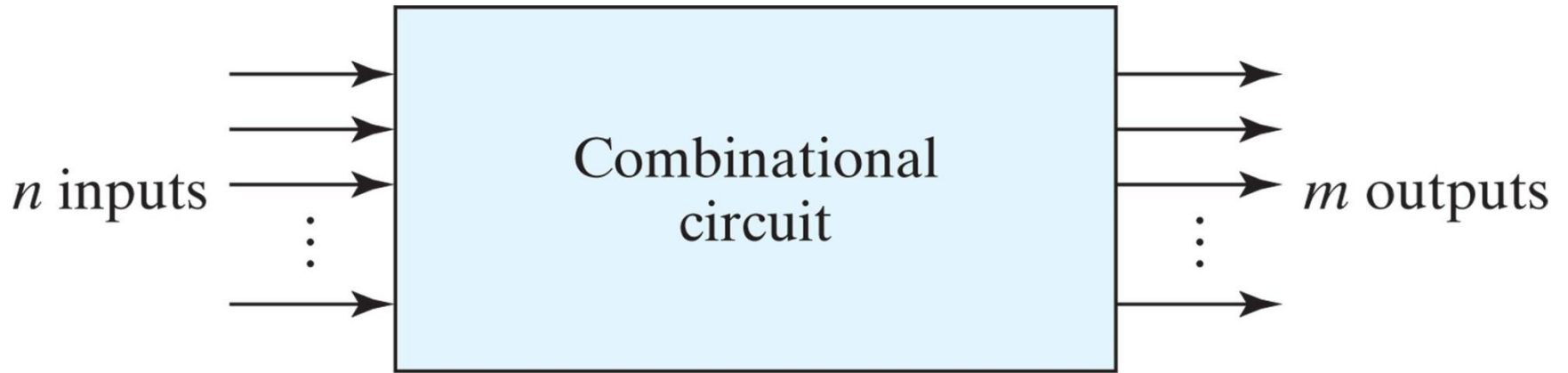


Chapter Four

Combinational Logic

- Two basic types of logic circuits
 - Combinational
 - Output(s) depend solely on the inputs
 - Sequential
 - Output(s) depend on inputs and a feedback mechanism.
 - More on sequential circuits in Chapter 5



For n inputs

2^n possible combinations

For each combination of inputs, there is
one possible value for each output variable.

Therefore, a combinational circuit can be
described by a

Truth Table.

Common Combinational Circuits


- Adders/subtractors
- Comparators
- Decoders
- Encoders
- Multiplexers.

Analysis of a given circuit

1. Make sure the circuit is combinational and not sequential.
 - No Feedback paths
 - No Memory elements
2. Obtain the Boolean functions or truth table applicable to the circuit.

Obtaining the Boolean Functions

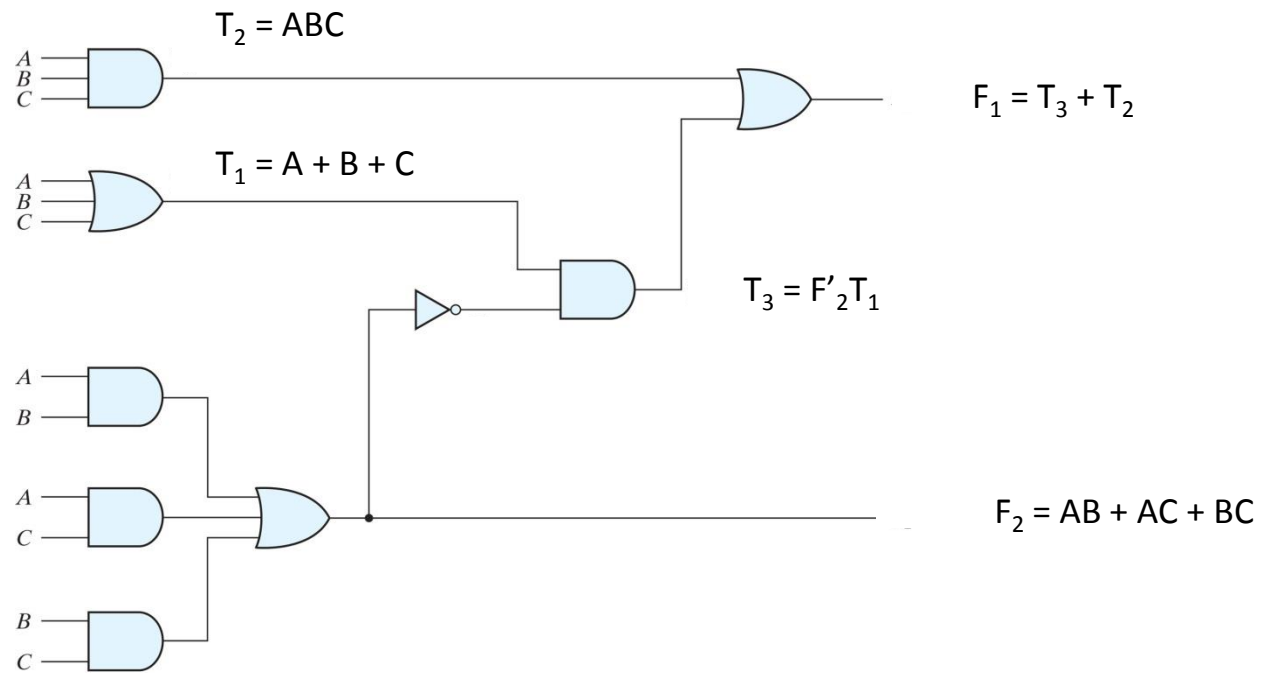1. Label all gate outputs that are a function of the inputs.
 - Labels are arbitrary, BUT
 - Names should be meaningful
2. Label the gates that are a function of input variables and/or previously labeled gates.
3. Repeat Step 2
4. Substitution



Substitution

$$F_1 = T_3 + T_2$$

$$F_1 = T_3 + T_2$$

$$T_3 = F'_2 T_1$$

$$T_2 = ABC$$

$$T_1 = A + B + C$$

$$F_2 = AB + AC + BC$$

And now derive the truth table

Table 4.1*Truth Table for the Logic Diagram of Fig. 4.2*

A	B	C	F₂	F'₂	T₁	T₂	T₃	F₁
0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	1	1	0	1	1
1	0	1	1	0	1	0	0	0
1	1	0	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1

Design

- Starts with a specification.
 1. Determine the number of required inputs.
 2. Derive the truth table.
 3. Obtain the simplified Boolean Functions.
 4. Implement the circuit.

Example Circuit

Need a circuit that takes 2 inputs and has 2 outputs.

When the inputs are both 0, the outputs are both zero.

When the inputs are both 1, the outputs are 1 and 0, respectively.

When the inputs are different, the outputs are 0 and 1 respectively.

- How many inputs are needed?
 - 2, let's call them x and y.
- How many outputs are needed?
 - 2, let's call them C and S
- Build the table.


x	y	C	S
0	0		
0	1		
1	0		
1	1		

- How many inputs are needed?
 - 2, let's call them x and y.
- How many outputs are needed?
 - 2, let's call them C and S
- Build the table.

x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$C = xy$$

$$S = xy' + x'y$$

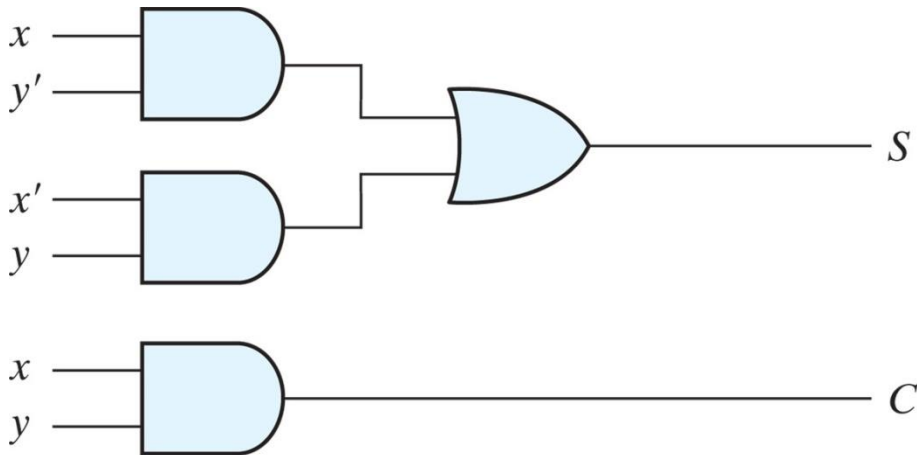


x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$C = xy$$

$$S = xy' + x'y$$


$$= x \oplus y$$

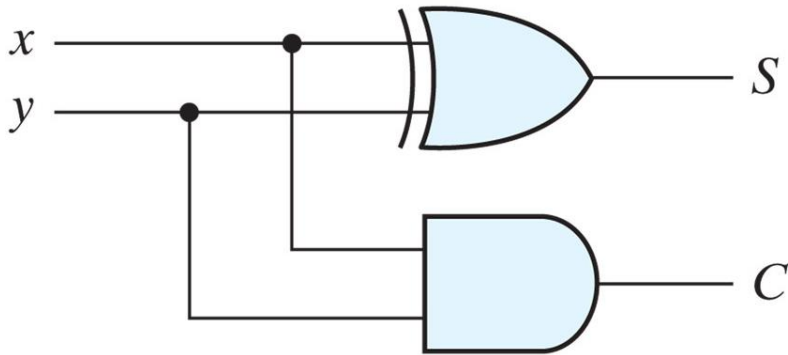

x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Half-Adder

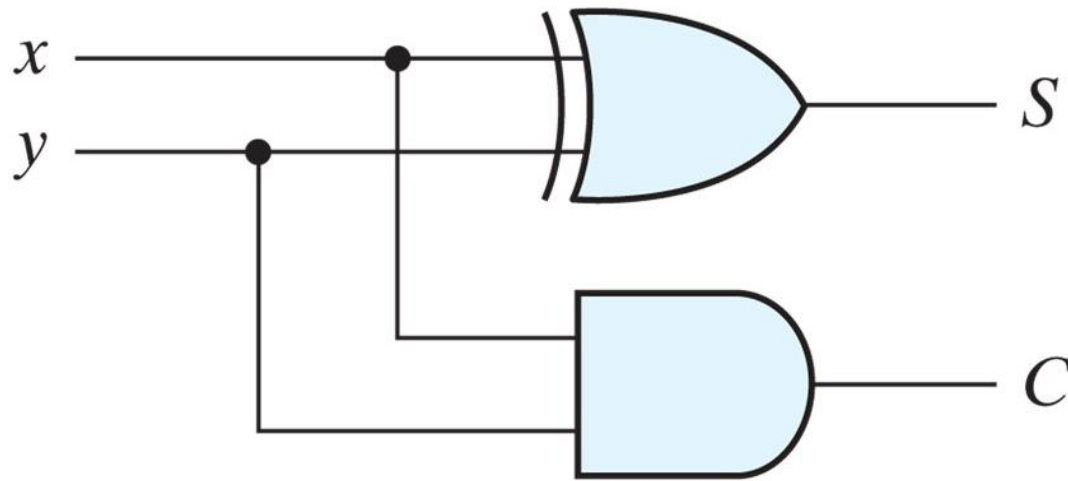A combinational circuit that performs the addition of two bits.



Full-Adder

Full Adder

<i>x</i>	<i>y</i>	<i>z</i>	<i>c</i>	<i>s</i>
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

Full-Adder

Full Adder

<i>x</i>	<i>y</i>	<i>z</i>	<i>c</i>	<i>s</i>
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Find the Boolean Functions

		y			
		00	01	11	10
x \ yz	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6
			1		1
		1		1	



(a) $S = x'y'z + x'yz' + xy'z' + xyz$

		y			
		00	01	11	10
x \ yz	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6
				1	
			1	1	1

(b) $C = xy + xz + yz$


Full Adder

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

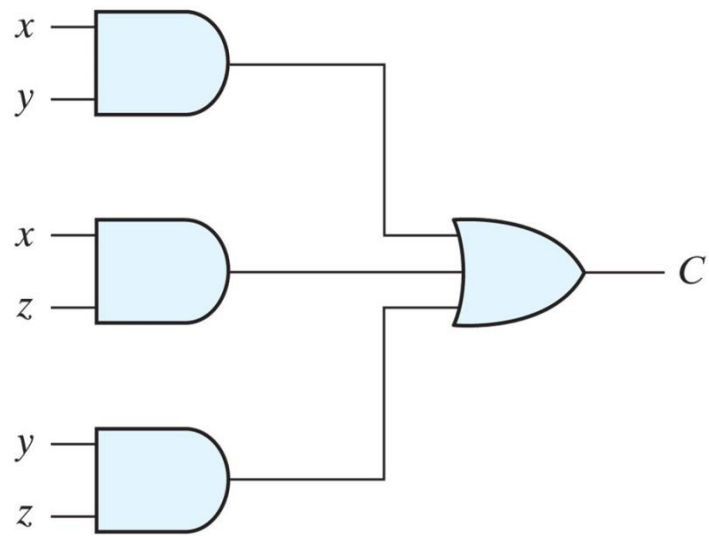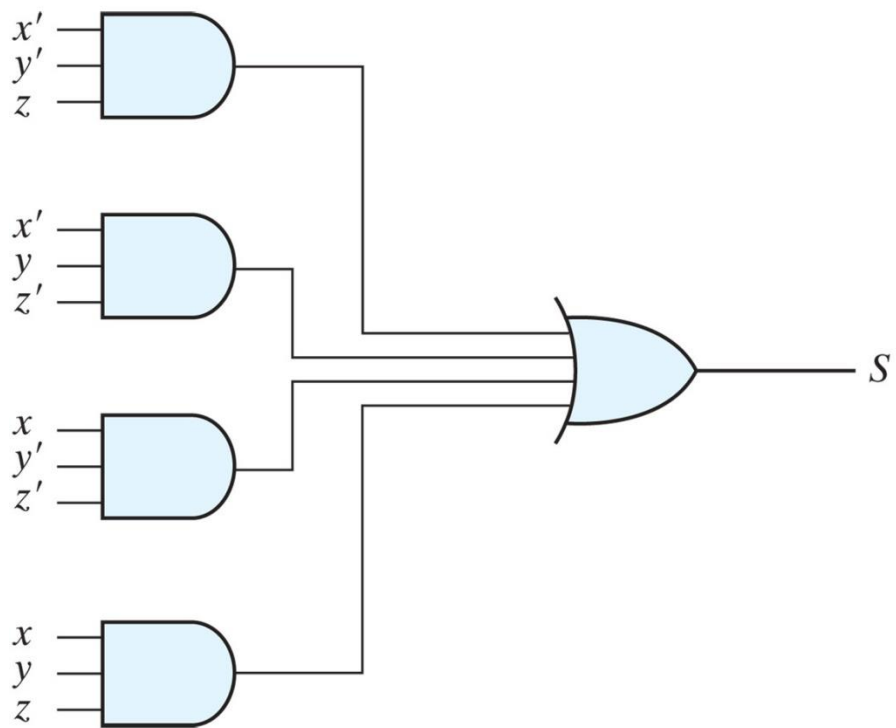

Further Examination

Further Examination

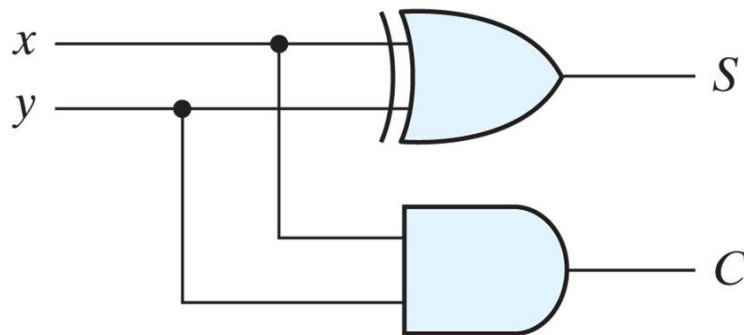


Full Adder

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0

Another implementation

Full Adder

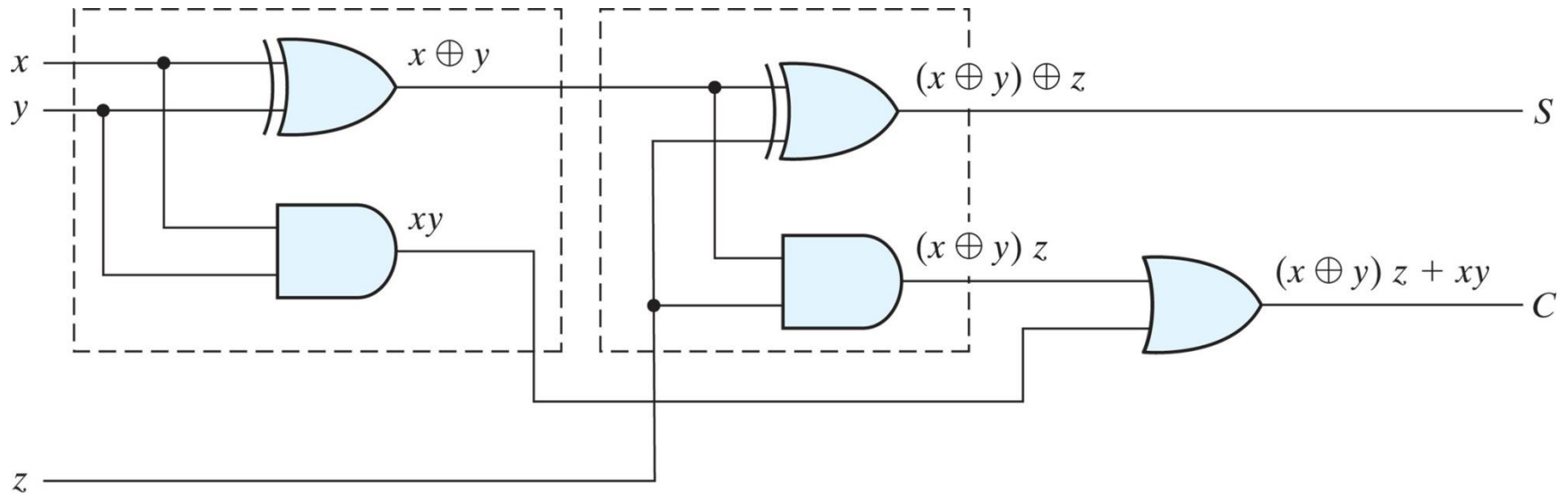

Binary Adder

- Provides the arithmetic sum of two binary numbers.
- n full adders cascaded
- OR 1 half-adder and $n-1$ full adders cascaded

Full-Adders Cascaded

