


Chapter 4

part 3

If asked to design a circuit

- Where to start
 - Truth table – based on requirements/specs
 - Required outputs – based on a timeline
- Build circuit
- Test circuit
- Does the output match the specifications?
 - Yes – done
 - No - redesign

Review

 

Decoder

- n to m
- m a max of 2^n
- Only one output active at any given time
- Can have an **Enable** input

Encoder

- Maximum of 2^n inputs and n outputs.
- Output tells you which input line is active



Priority Encoder


- Still Encodes
- If two or more inputs are active at any given time, the highest priority one gets attention.

Table 4.8
Truth Table of a Priority Encoder

Inputs				Outputs		
D_0	D_1	D_2	D_3	x	y	V
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

Maps for Priority Encoder

 
 


 


Multiplexer

- Selects an input and directs it to the output.
- The selection is made via « selection lines »
 - 2^n input lines (normally)
 - n selection lines
 - 1 output

Basic Circuit and Logic Symbol

  


S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

 


Synthesis of a Logic Function

w_1	w_2	f
0	0	0
0	1	1
1	0	1
1	1	0

 

Synthesis of a Logic Function

w_1	w_2	f		w_1	f
0	0	0	}	0	w_2
0	1	1			\bar{w}_2
1	0	1	}	1	
1	1	0			

 

x	y	z	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

x	y	z	F	
0	0	0	0	$F = z$
0	0	1	1	
0	1	0	1	$F = z'$
0	1	1	0	
1	0	0	0	$F = 0$
1	0	1	0	
1	1	0	1	$F = 1$
1	1	1	1	

